



Electronics Overview



Outline

-
- Electronics Overview
 - Op-Amp Circuits
 - Analog Filters
 - Analog to Digital
 - Electrical Lab Instruments
 - Project Introduction RLC Circuit Control

Electronics Overview

Electrical Units

- Voltage: volts ($\mu\text{v} \rightarrow \text{kv}$)
- Current: amperes (amps), milliampere ($\text{ma } 10^{-3}$), microampere ($\mu\text{a } 10^{-6}$)
- Resistance: ohms Ω , k-ohms ($\text{k } 10^3$), meg ohms ($\text{m } 10^6$)
- Capacitance: farad, microfarad ($\mu\text{f } 10^{-6}$), nanofarad ($\text{nf } 10^{-9}$), picofarad ($\text{pf } 10^{-12}$)
- Inductance: henry, millihenry, microhenry
- Frequency: mhz, ghz 10^9

Electronics Overview

Fingertip Facts

volts \Leftrightarrow kohms \Leftrightarrow milliamperes

khz $10^3 \Leftrightarrow 10^{-3}$ = milliseconds

mhz $10^6 \Leftrightarrow 10^{-6}$ = microsecond

ghz $10^9 \Leftrightarrow 10^{-9}$ = nanosecond

60hz \Leftrightarrow 16.3 millisecond period

capacitance \Leftrightarrow μf 10^{-6} , nf 10^{-9} , pf 10^{-12} (pico), 10^{-15} (femtofarad)

seconds = mohm (resistance) x μf (capacitance)

$2^{10} \Leftrightarrow 1023$

$\omega = 2\pi f$

3dB \Leftrightarrow half power point

$$dB = 20 \log \left(\frac{V_o}{V_i} \right) \quad dB = 10 \log \left(\frac{P_o}{P_i} \right)$$

Electronics Overview


Electrical Symbols




ground



resistor, variable

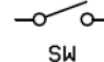

spst

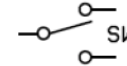

spdt
switches




dpdt




capacitor



Inductor

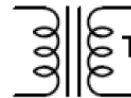

transformer

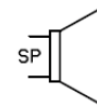

speaker



fuse



npn, pnp




diode zener diode



mosfets

Electronics Overview

Kirchhoff's Laws

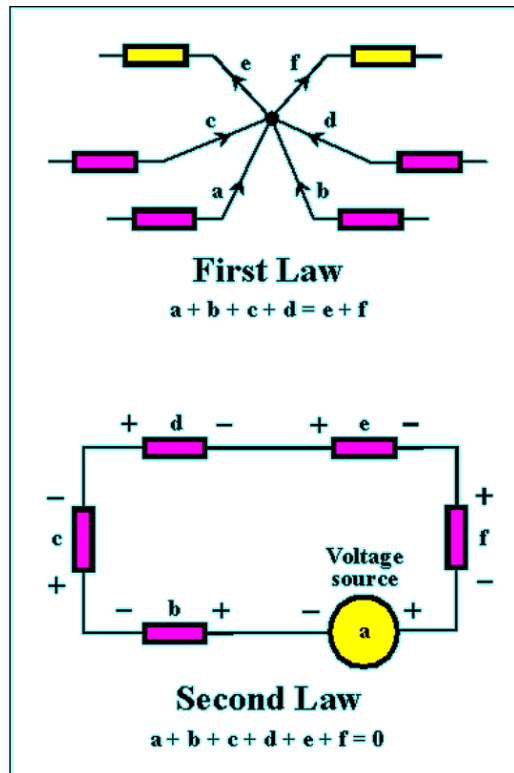

1st Kirchhoff's Law (KCL)

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

2nd Kirchhoff's Law (KVL)

$$\sum \xi = \sum IR$$


Electronics Overview

Basic Electrical Components: Resistors

- $V=IR$
- Resistor parameters: resistance, tolerance and power rating.
- Variable resistors: pots
- Resistors are color coded
- Standard values (10%)
 - 10 12 15 18 22 27 33 39 47 56 68 82
- Common tolerance: $\pm 5\%$, $\pm 2\%$, $\pm 1\%$
- Series/parallel combination
- Why is high value used in power lines?

Electronics Overview

Basic Electrical Components: Resistors

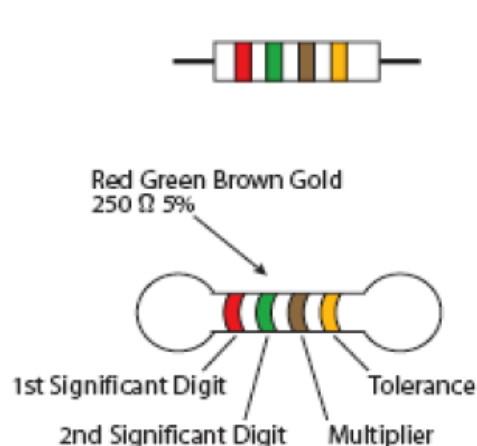


Color	1st-band Digit	2nd-band Digit	3rd-band Digit	4th-band Digit
Black	0	0	$10^0 - 1$	
Brown	1	1	$10^1 - 10$	1%
Red	2	2	$10^2 - 100$	2%
Orange	3	3	$10^3 - 1000$	3%
Yellow	4	4	$10^4 - 10000$	4%
Green	5	5	$10^5 - 100000$	
Blue	6	6	$10^6 - 1000000$	
Violet	7	7	$10^7 - 10000000$	
Gray	8	8	$10^8 - 100000000$	
White	9	9	$10^9 - 1000000000$	
Gold				5%
Silver				10%
None				20%

Figure by MIT OpenCourseWare.

red green brown gold
2 5 0 Ω 5%

Electronics Overview

Basic Electrical Components: Capacitors

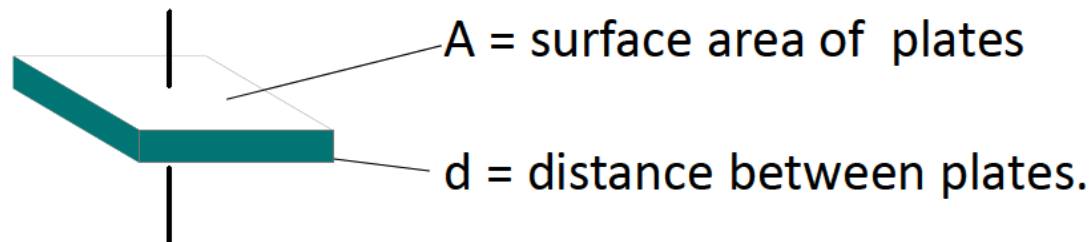

$$C = \frac{K\epsilon_0 A}{d} \quad Z = \frac{1}{sC} \quad i = C \frac{dv}{dt} \quad i \downarrow \frac{1}{C} \quad \begin{matrix} + \\ v \\ - \end{matrix}$$

Standard Capacitance Values: 10 12 15 18 22
27 33 39 47 56 68 82

Examples: 100pf, 180pf, 270pf,... 1μf , 2.2μf , 4.7μf ,...

Capacitor marking: 104 = 10×10^4 pf = $10^5 \times 10^{-12}$ f = 10^{-7} f = 0.1 μf

Electronics Overview

Basic Electrical Components: Capacitors

- Parallel / Series combination
Think!



- Capacitors range for 1 pf (10^{-12}) to 100,000 μf (10^{-1})
- Typically capacitors larger than 1 μf are polarized. Non polarized units are marked NP (non-polar) or BP (bipolar).
- All capacitors have maximum voltage ratings.

Electronics Overview

Basic Electrical Components: Capacitors




Electronics Overview

Basic Electrical Components: Inductors

$$v(t) = L \frac{d}{dt} i(t)$$

$$Z = sL$$

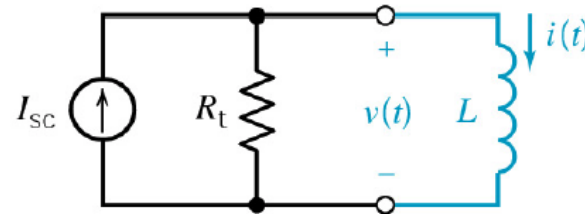


- Inductors are used in tuned circuits, switching power supplies, voltage converters, light dimmers, GFI.
- Inductors vary from a few μh (etched on a pcb) to henries.

Electronics Overview


Basic Electrical Components: Diode

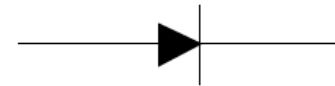- Diodes allow current to flow in the direction of the arrow.
- Can be modeled as an open circuit in one direction and a short circuit in the other (with a 0.6 volt drop)
- Diode parameters: max current, reverse breakdown voltage, reverse recovery time.



Electronics Overview

Basic Electrical Components: Transistor

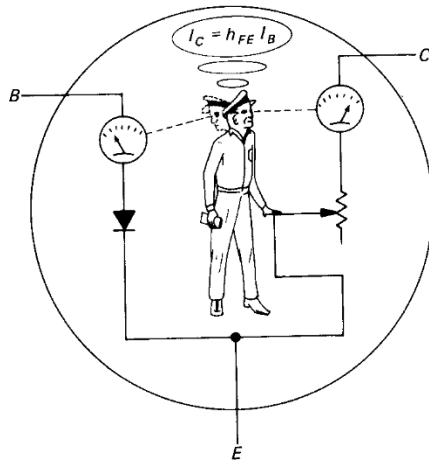

Thank You, Transistor Man!

A low base current (gate voltage) controls a much larger collector (drain) current

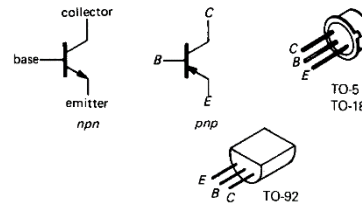


Figure 2.1. Transistor symbols, and small transistor packages.


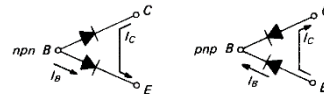


Figure 2.2. An ohmmeter's view of a transistor's terminals.

$$I_C = h_{fe} i_B = \beta i_B$$

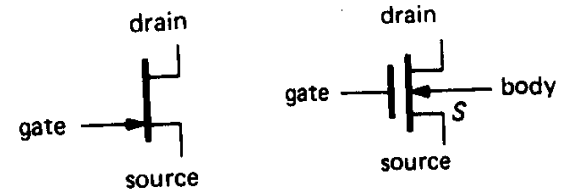


$$I_s = g_m V_{gs}$$

Transconductance


Electronics Overview

Diode and Transistor

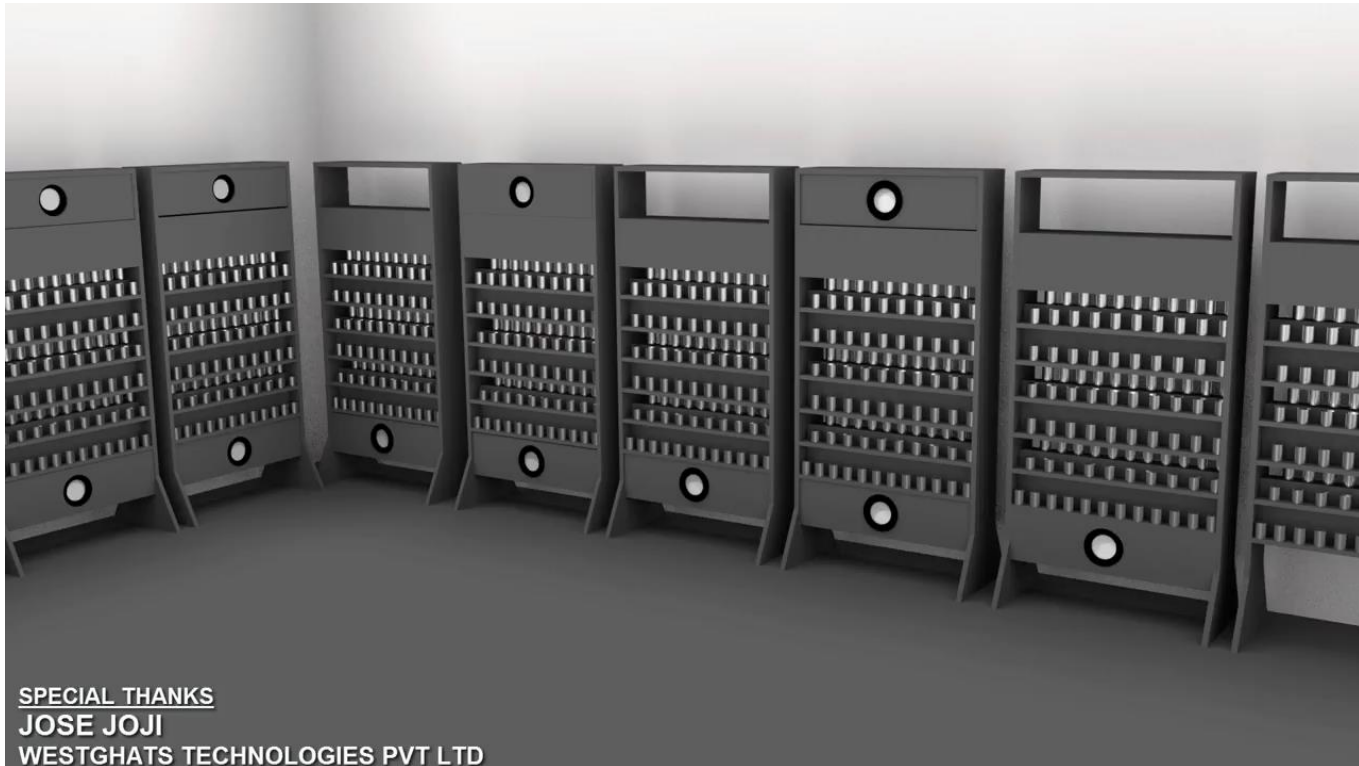


Electronics Overview

Bipolar Junction Transistor

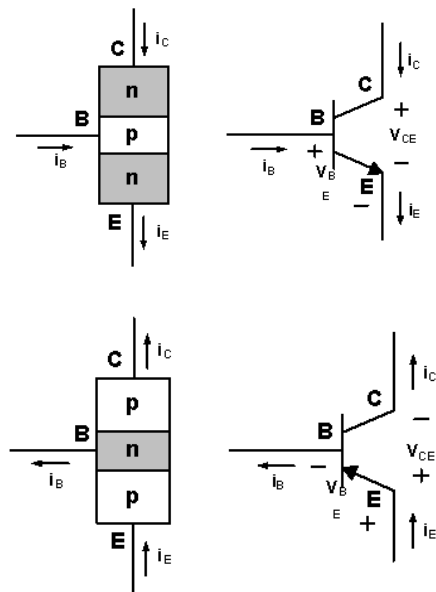


Emitter Base Collector

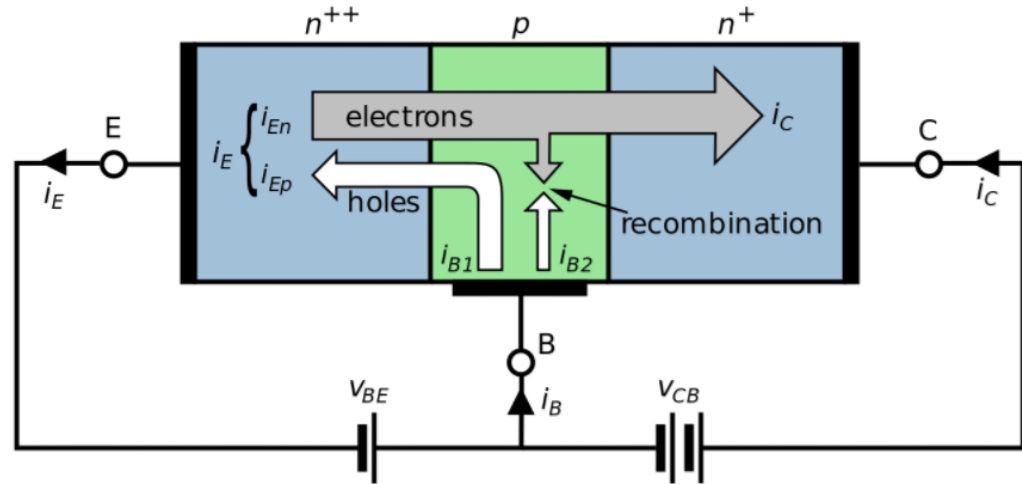

Emitter and base has forward bias
Thin base layer for minority carrier


Electronics Overview

Field Effect Transistor

 

Op-Amp Circuits

“Ideal” OpAmp Model

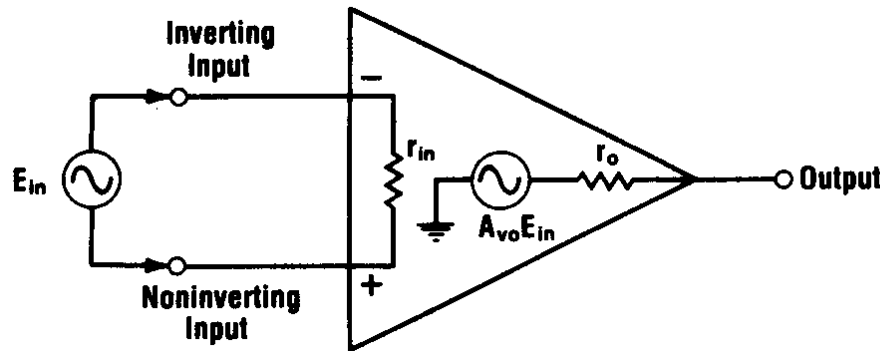

$$E_o = A_{vo} E_{in}$$

$$A_{vo} = \infty$$

$$r_{in} = \infty$$

$$r_o = 0$$

$$BW = \infty$$


$$E_o = 0 \text{ if } E_{in} = 0$$

Fig. 1-1. Equivalent circuit for an ideal operational amplifier.

1. The voltage gain is infinite— $A_{vo} = \infty$.
2. The input resistance is infinite— $r_{in} = \infty$.
3. The output resistance is zero— $r_o = 0$.
4. The bandwidth is infinite— $BW = \infty$.
5. There is zero input offset voltage— $E_o = 0$ if $E_{in} = 0$.

Op-Amp Circuits

Comparator

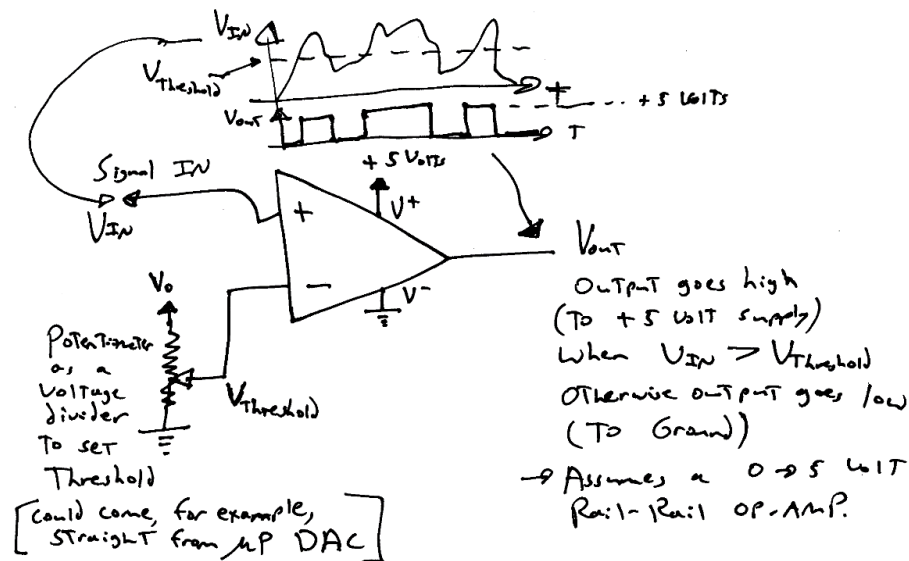


Makes an analog signal into a 1-bit digital signal

- Directly drives logic pin on microprocessor
- Detects when signal is above threshold

Op-Amp Circuits

Voltage-Follower/Buffer

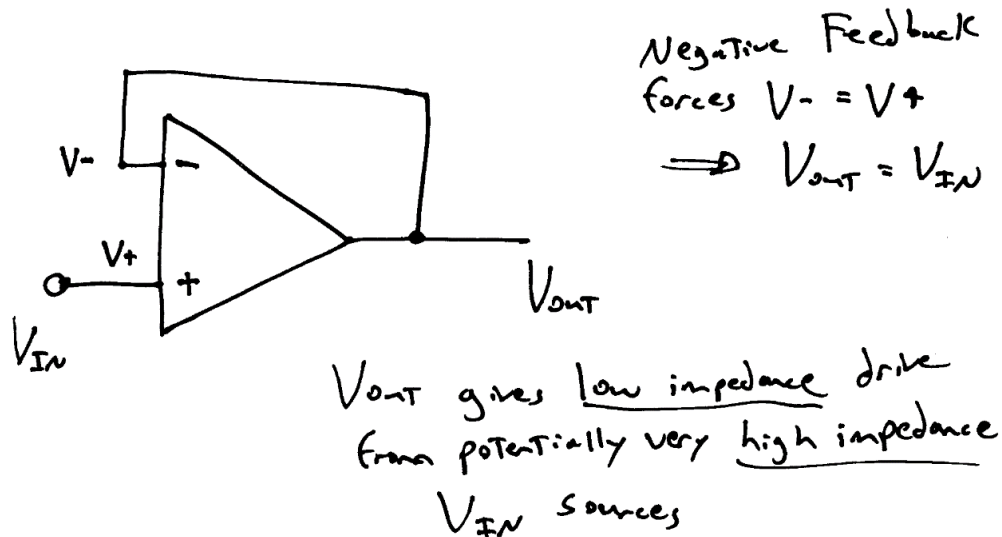


A unity-gain buffer to enable high-impedance sources to drive low-impedance loads

Op-Amp Circuits

Non-Inverting Amplifier

Like voltage follower, but gives voltage gain

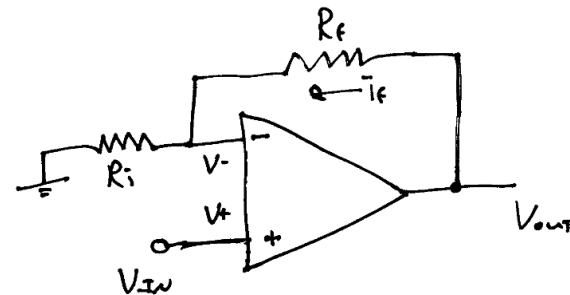- Gain can be adjusted from unity upward via resistor ratio
- High-Z input is good for conditioning High-Z sensors



Again, negative feedback means $V_- = V_+$ when the OpAmp is working.

Non-inverting OP-Amp gives Low-Z V_{OUT} from very high-Z V_{IN} , But also offers Voltage Gain $\Rightarrow 1 + R_f/R_i$

$$V_- = V_{OUT} \left(\frac{R_i}{R_f + R_i} \right) = V_+ = V_{IN}$$


Voltage Divider!

$$\therefore V_{OUT} = V_{IN} \left(\frac{R_f + R_i}{R_i} \right) = V_{IN} \left(1 + \frac{R_f}{R_i} \right)$$

Gain

Op-Amp Circuits

Transimpedance Amplifier

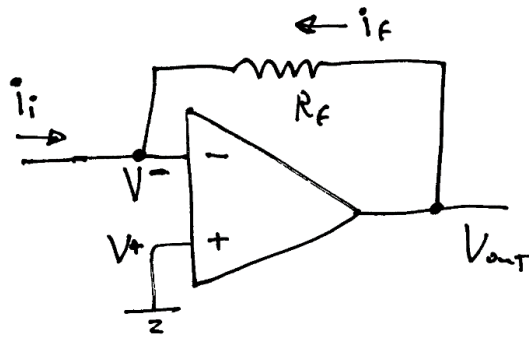

V_{out} gives good
low- z drive
(low impedance)


$Z_{in} \rightarrow \infty$
means
 $i_i = -i_f = -\frac{V_{out}}{R_f}$
Negative Feedback forces
 $V^- = V^+$
 $\therefore V_{out} = -i_i R_f$

Converts a current into a voltage

- Generates a proportional (w. R_f) voltage from an input current
- Produces a low-impedance output that can drive a microcomputer's A-D converter, for example

Op-Amp Circuits

Inverting Amplifier

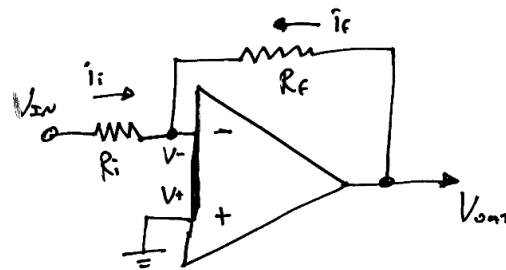

Inverting Op Amp
 produces negative
 voltage gain : $-\frac{R_f}{R_i}$
 Input Impedance = R_i
 (not huge, as with inverting Op Amp)


$$\begin{aligned} i_f &= -i_i, \text{ since } Z_{in} \rightarrow \infty \\ V_+ &= V_- = 0, \text{ because of negative feedback and grounded } V_+ \\ \Rightarrow i_f &= \frac{V_{out}}{R_f} = -i_i = \frac{V_{in}}{R_i} \\ V_{out} &= V_{in} \underbrace{\left(-\frac{R_f}{R_i}\right)}_{\text{Gain}} \end{aligned}$$

Inverts signal, voltage gain varies from zero upward with the ratio of two resistors

- Extension to summer is trivial with additional R_i 's
- Input impedance is not infinite: $Z_{in} = R_i$

Op-Amp Circuits


Adder

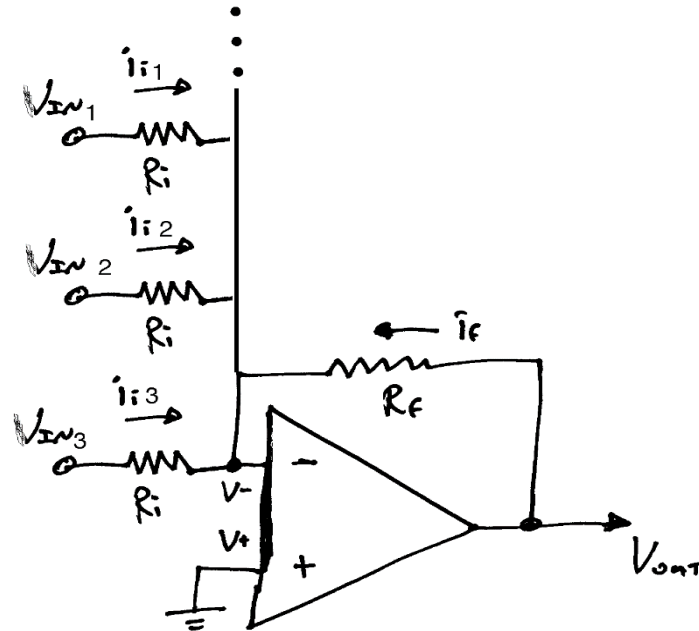

No crosstalk between inputs because of virtual ground

Op-Amp Circuits

Differential Amplifier

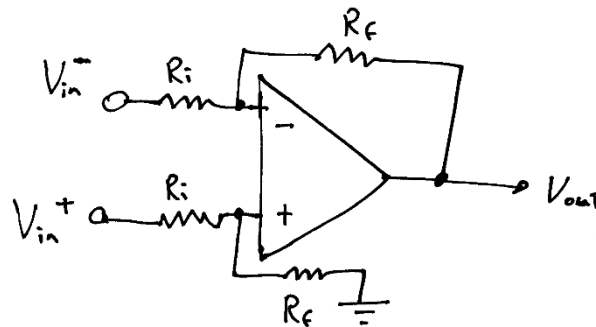

Voltage Gain \rightarrow

$$V_{out} = (V_{in}^+ - V_{in}^-) \frac{R_f}{R_i}$$

$$Z_{in}^- = R_i$$

$$Z_{in}^+ = R_i + R_f$$

\Rightarrow Unequal $Z_{in} \rightarrow$ Unbalanced

Subtracts two input signals


- Input resistors must be equal, feedback and shunt resistors must be equal
- Provides voltage gain

The input impedances aren't equal, however

- The amplifier is *unbalanced*!
 - A high-impedance sensor will produce common-mode errors (e.g., the system will be sensitive to the common voltage)
 - Differential sensors will be more sensitive to induced pickup signals (which tend to be high impedance)

Op-Amp Circuits

Basic Instrumentation Amplifier

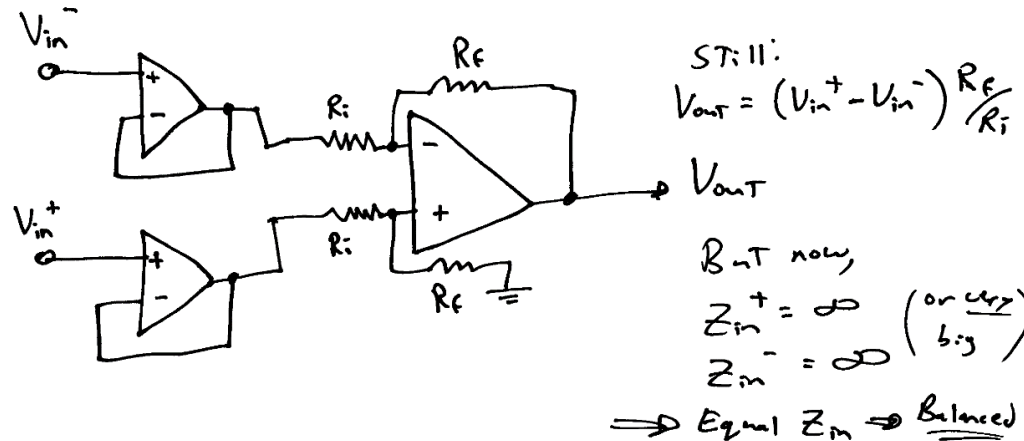


Buffer each leg of the differential amplifier by a voltage follower

- Impedance is now extremely high at both inputs
- Impedance can be set by a shunt resistor across inputs
- This is a *balanced* “instrumentation” amplifier

Op-Amp Circuits

Three-Op-Amp Instrumentation Amplifier

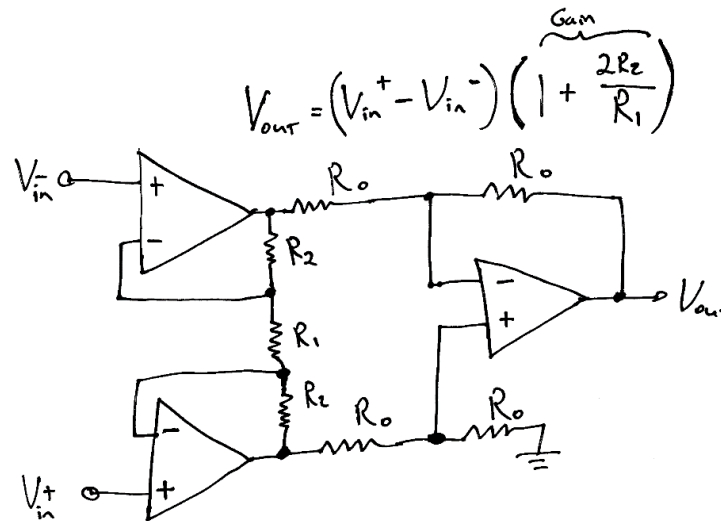

Gain is varied by changing only one resistor, R_1

- No need to re-trim other components for a gain change
- Gain at first stages is better for signal/noise
- This is the instrumentation amplifier of choice

Analog Filters

Passive RC Filters

- Passive LP Filter: RC network: $f_c = 1/(2\pi RC)$

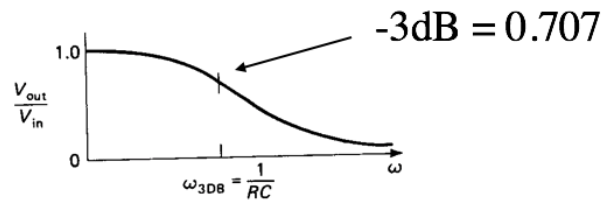
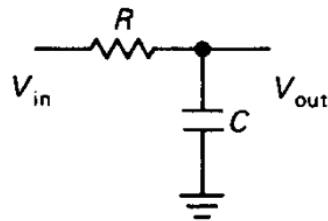


Figure 1.59. Frequency response of low-pass filter.

- Passive HP filter: RC network: $f_c = 1/(2\pi RC)$


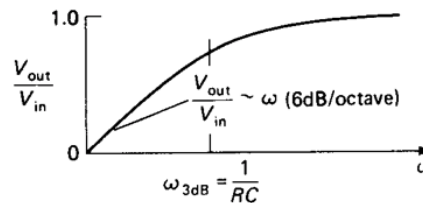
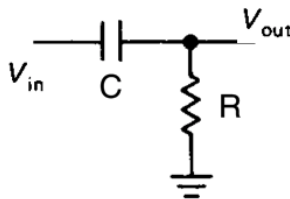
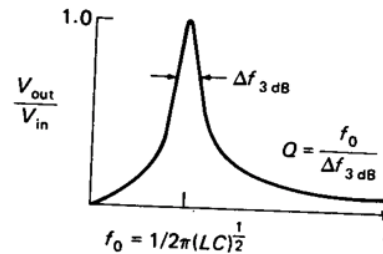


Figure 1.55. Frequency response of high-pass filter.

Analog Filters

Passive RLC Filters

- Resonant parallel RLC bandpass filters


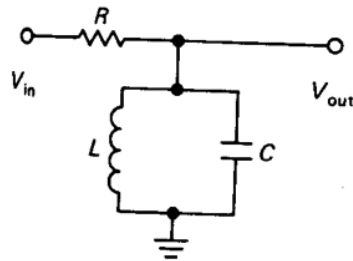


$$Q = \omega_0 RC$$

$$= f_0 / \Delta f_{3dB}$$

$$Z_{LC} \rightarrow \infty @ f_0$$

- Resonant series RLC notch filters

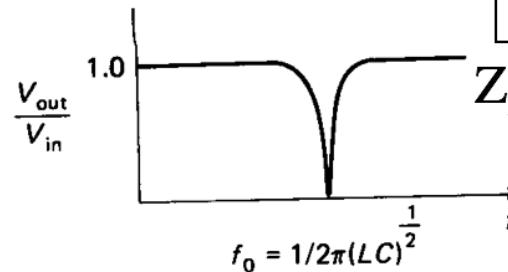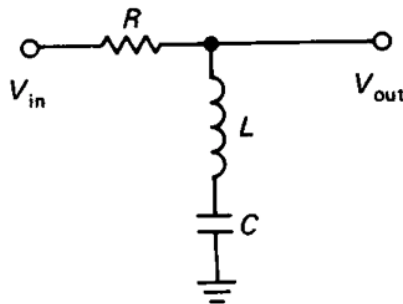


$$Q = \omega_0 (L/R)$$

$$= f_0 / \Delta f_{3dB}$$

$$Z_{LC} \rightarrow 0 @ f_0$$


Analog Filters

Active Filters: Differentiator

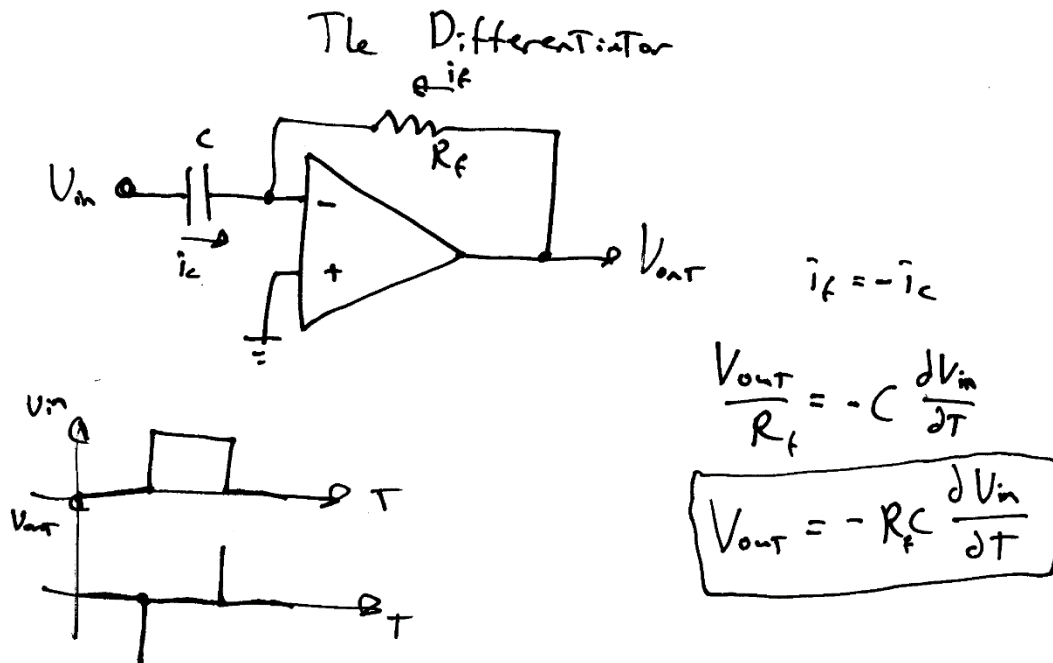

Analog Filters

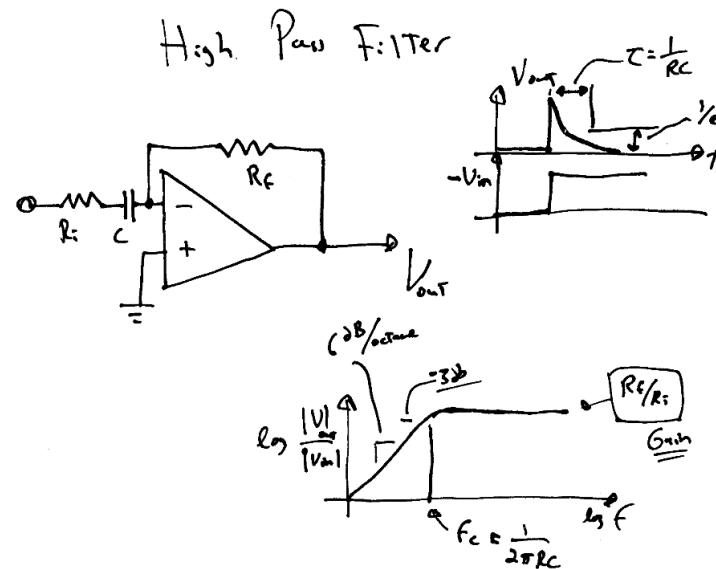Active Filters: First-order Active High Pass Filter




Low impedance drive

Voltage gain via R_f/R_i

Analog Filters


Active Filters: Integrator

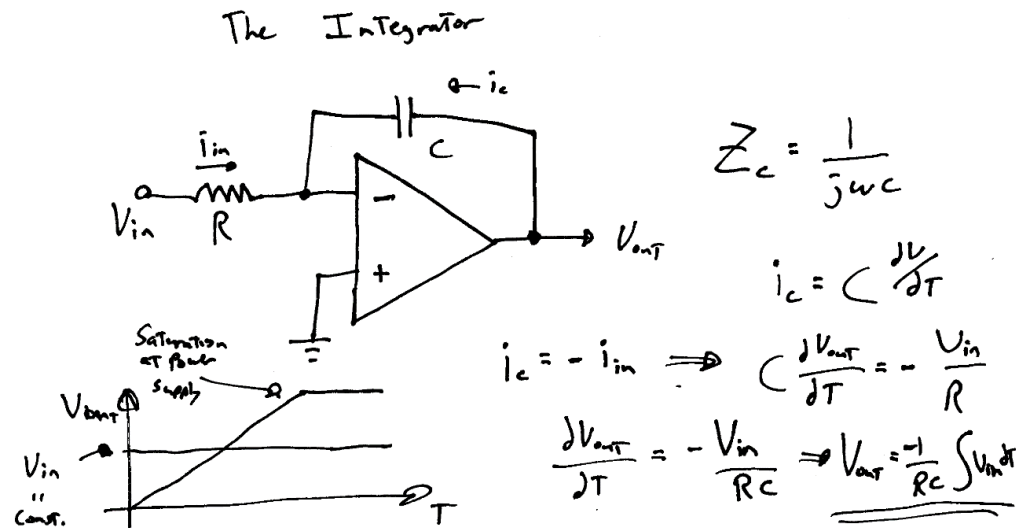

Saturates at rail!!

Analog Filters

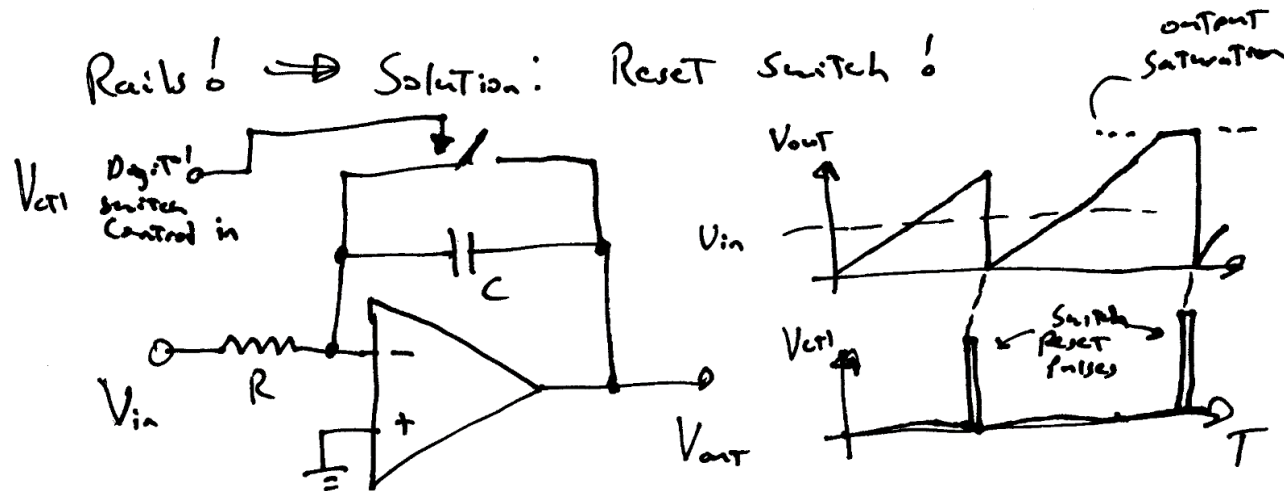Active Filters: Integrator with Reset Switch




Electronic switch in feedback forces output to ground when closed

- Discharges capacitor
- Resets Integrator!


Analog Filters

Active Filters: First-Order Active Low Pass Filter

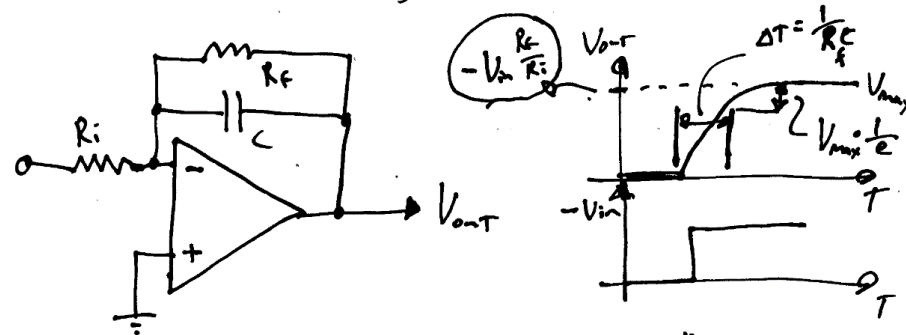The Leaky Integrator \rightarrow Low Pass Filter




Low impedance
output !!
Voltage gain !!

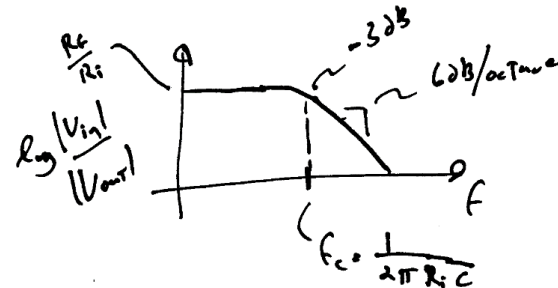

Analog Filters

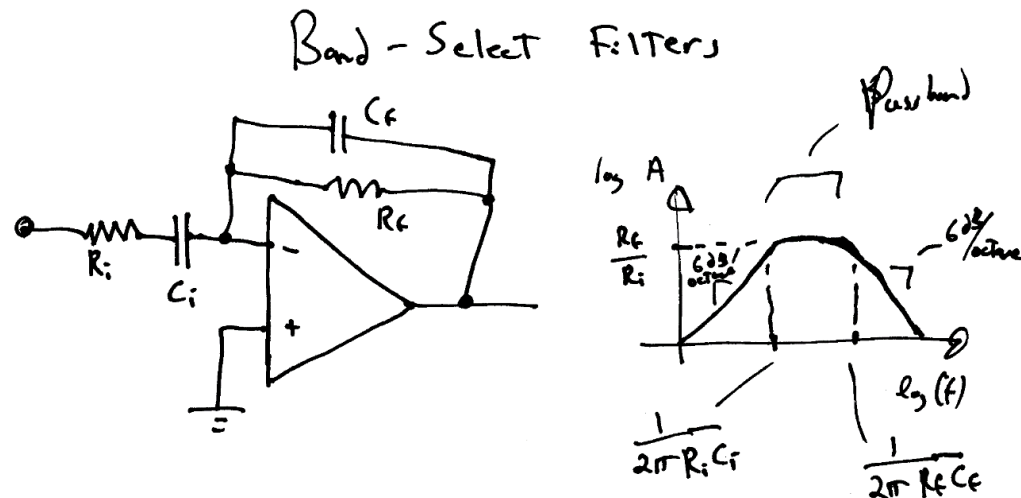Active Filters: First-Order Active Band Pass Filter





Cascaded high and low pass filters

- Always follow high-pass with low-pass (noise)
 - Low-Pass cutoff needs to be below high-pass cutoff!
- No Q, first-order rolloffs




Analog Filters

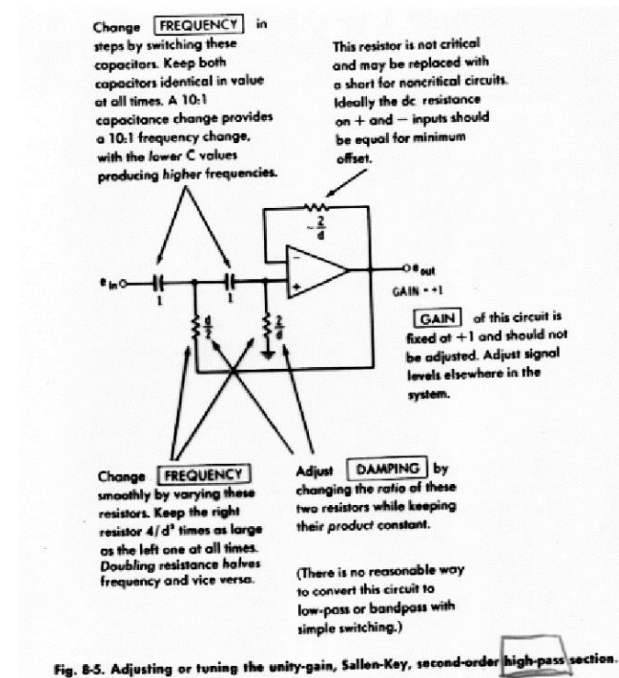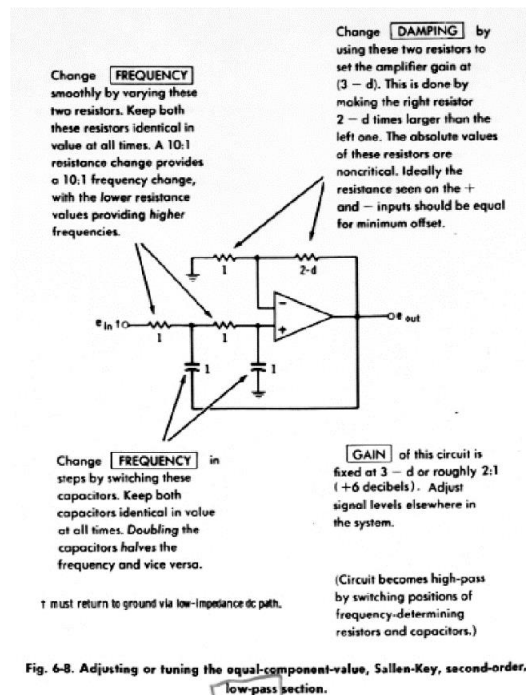Active Filters: Second-Order Filters (Sallen-Key Filters)



VCVS Filters

Analog to Digital Sampling

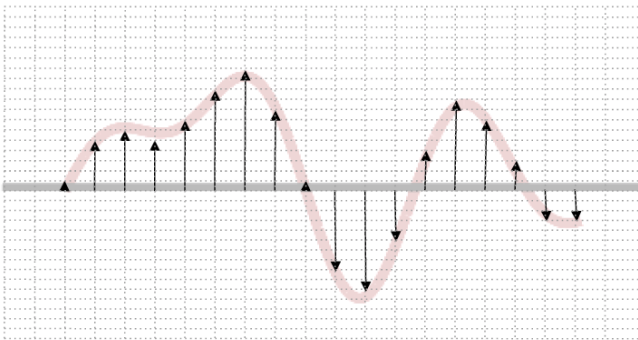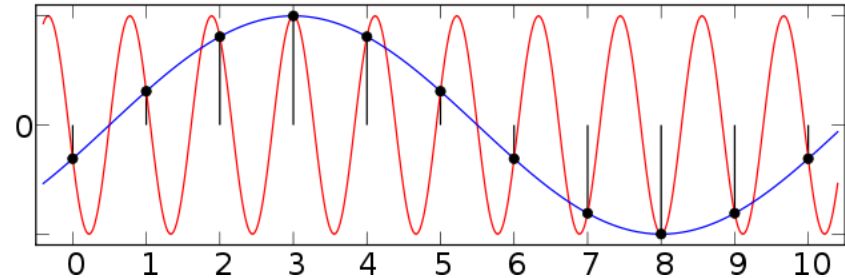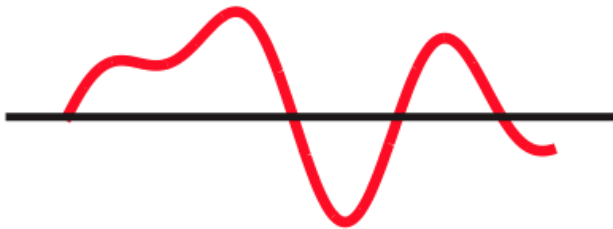

Nyquist Sampling Theorem

$$f_{in} < f_s/2$$


$$2f_{in} < f_s$$

Analog to Digital

Quantization

If we use N bits to encode the magnitude of one of the discrete-time samples, we can capture 2^N possible values.

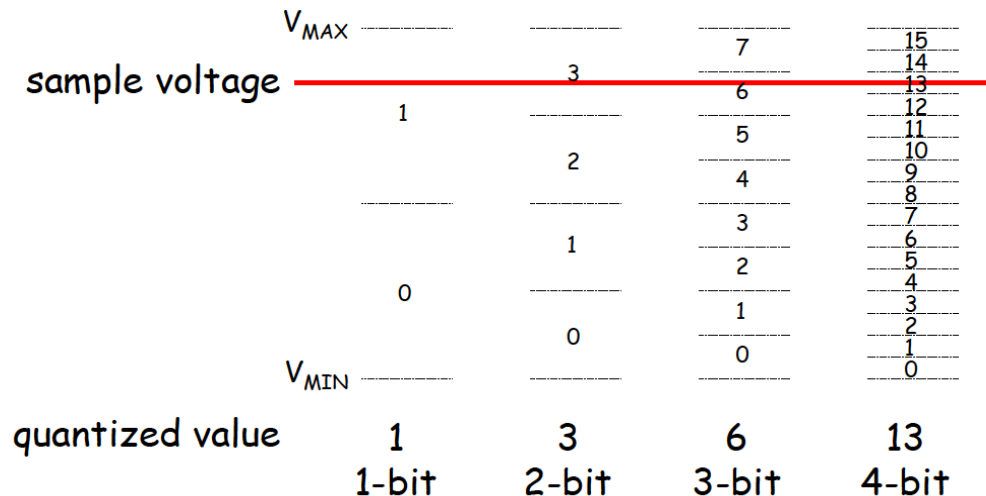
So we'll divide up the range of possible sample values into 2^N intervals and choose the index of the enclosing interval as the encoding for the sample value.




Analog to Digital

Signal-to-Noise Ratio (SNR)

$$SNR = 10 \log_{10} \left(\frac{P_{SIGNAL}}{P_{NOISE}} \right) = 10 \log_{10} \left(\frac{A_{SIGNAL}^2}{A_{NOISE}^2} \right) = 20 \log_{10} \left(\frac{A_{SIGNAL}}{A_{NOISE}} \right)$$

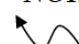 RMS amplitude

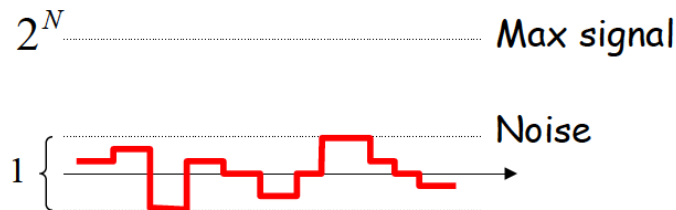SNR is measured in decibels (dB). Note that it's a logarithmic scale: if SNR increases by 3dB the ratio has increased by a factor 2. When applied to audible sounds: the ratio of normal speech levels to the faintest audible sound is 60-70 dB.




$$SNR = 20 \log_{10} \left(\frac{A_{signal}}{A_{noise}} \right) \approx 20 \log_{10} (2^N)$$

$$\approx N \cdot 6.02 dB$$


Electrical Lab Instruments

Breadboard

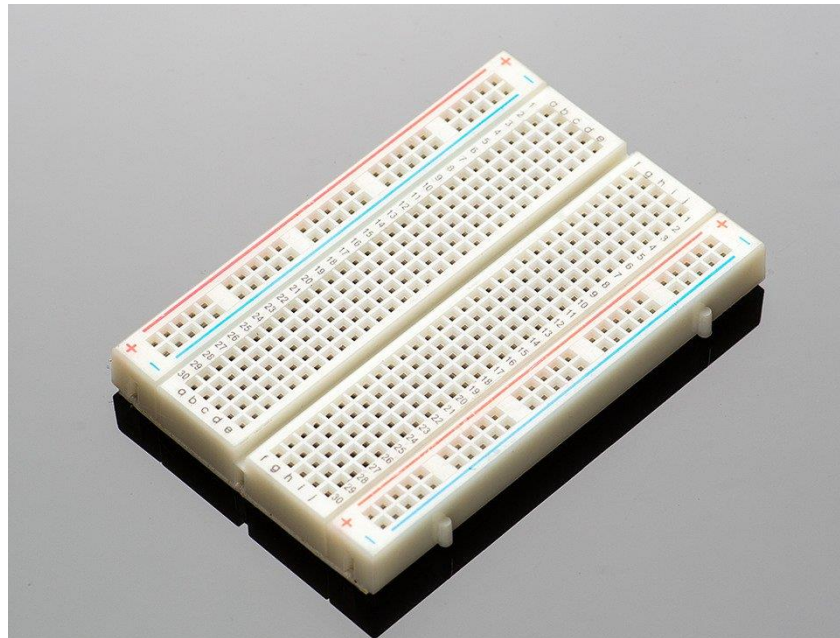

Electrical Lab Instruments

Protoboard

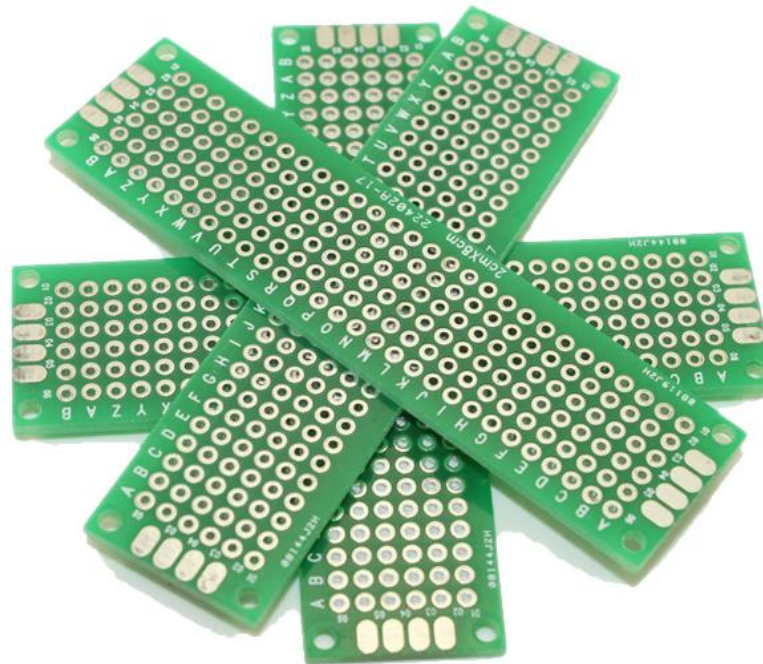


Electrical Lab Instruments

Multimeter




Electrical Lab Instruments

Soldering

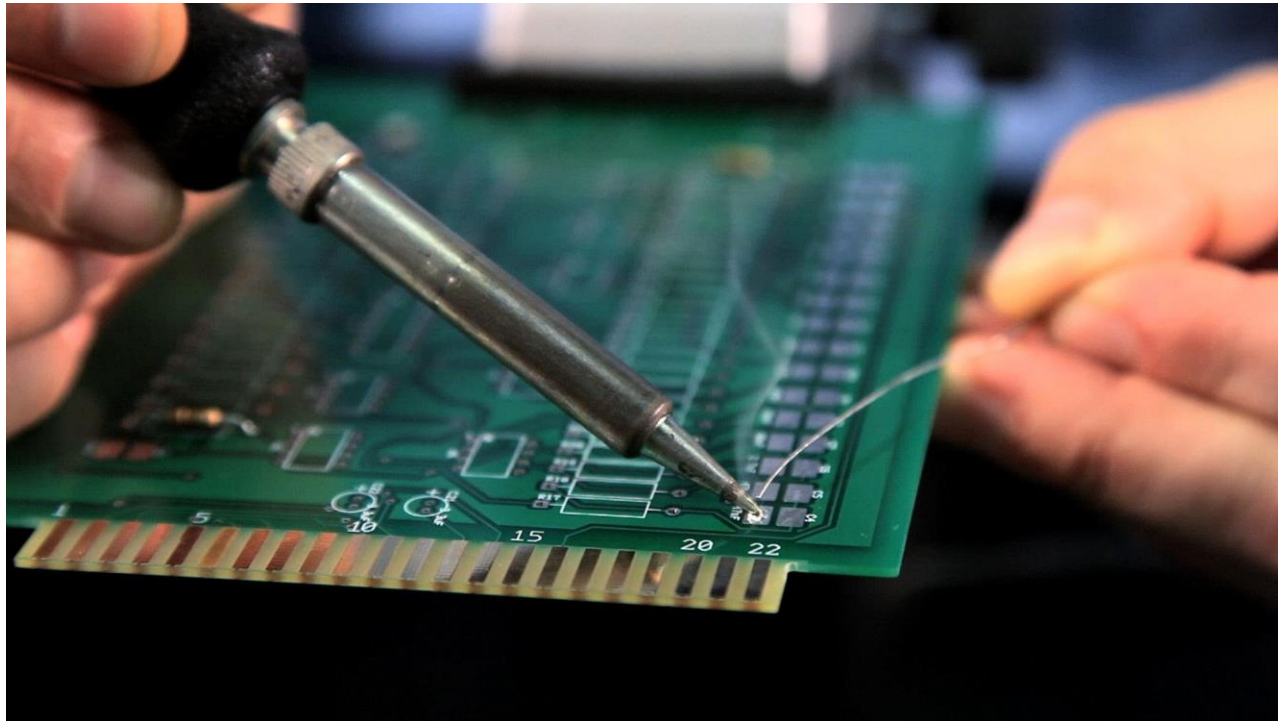

Electrical Lab Instruments

Oscilloscope

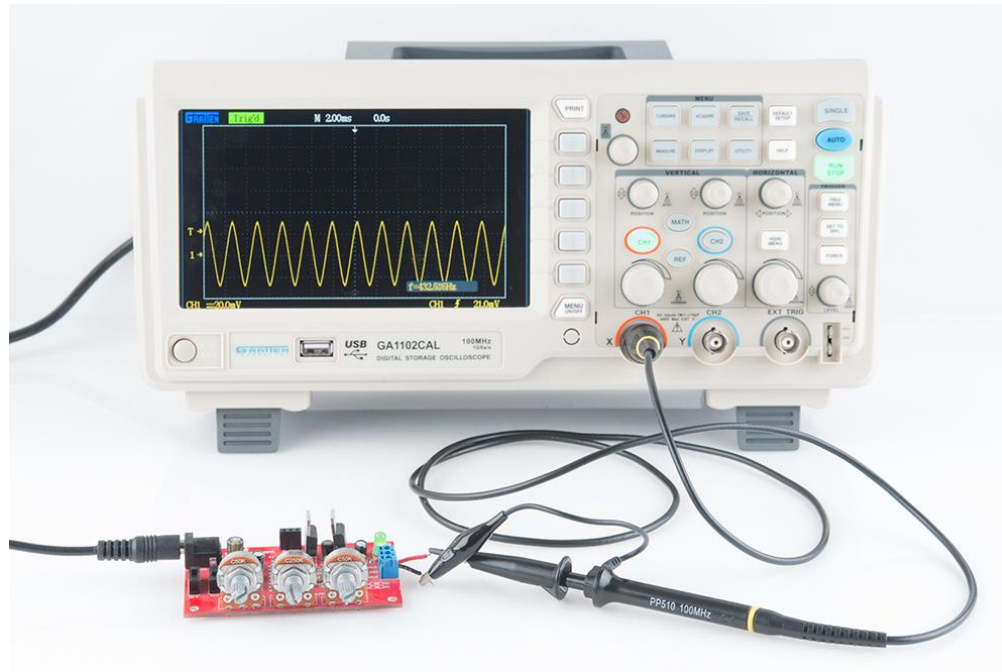



Caution!


**A big wave of mathematical definition
and manipulation is coming.**



System Identification

Goal of System Identification

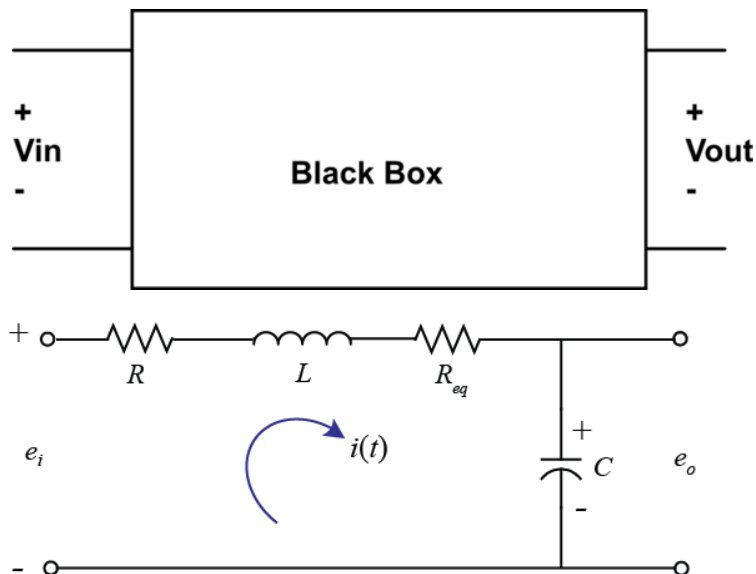- Obtain system characteristics when isolated component measurement is not possible
- Usually presented as frequency response for design purpose



$$e_i - iR - L \frac{di}{dt} - iR_{eq} - \frac{1}{C} \int i dt = 0$$

$$E_i(s) - I(s)R - LsI(s) - I(s)R_{eq} - \frac{1}{Cs}I(s) = 0$$

$$I(s) = \frac{E_i(s)}{R + Ls + R_{eq} + \frac{1}{Cs}}$$

$$\frac{E_i(s)}{R + Ls + R_{eq} + \frac{1}{Cs}} = \frac{E_o(s)}{\frac{1}{Cs}}$$

$$G(s) = \frac{E_o(s)}{E_i(s)} = \frac{\frac{1}{Cs}}{R + Ls + R_{eq} + \frac{1}{Cs}}$$

$$G(s) = \frac{\frac{1}{CL}}{s^2 + \frac{R+R_{eq}}{L}s + \frac{1}{CL}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\frac{1}{CL}} \quad \sigma = \zeta\omega_n = \frac{R + R_{eq}}{2L} \quad \zeta = \frac{\sigma}{\omega_n} = \frac{R + R_{eq}}{2} \sqrt{\frac{C}{L}}$$

System Identification

Complex Number and Taylor Series Review

- Real and imaginary parts
- Euler's formula

$$e^{ix} = \cos x + i \sin x$$

- Can be expressed with magnitude and phase

$$z = r(\cos \varphi + i \sin \varphi)$$



- Rules of multiplication and division

$$z_1 z_2 = r_1 r_2 (\cos(\varphi_1 + \varphi_2) + i \sin(\varphi_1 + \varphi_2))$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} (\cos(\varphi_1 - \varphi_2) + i \sin(\varphi_1 - \varphi_2))$$

- Taylor series definition
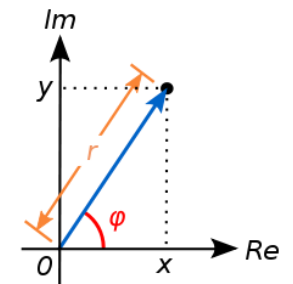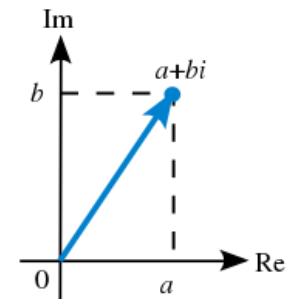
$$\sum_{n=0}^{\infty} \frac{f^{(n)}(a)}{n!} (x-a)^n = f(a) + \frac{f'(a)}{1!} (x-a) + \frac{f''(a)}{2!} (x-a)^2 + \frac{f'''(a)}{3!} (x-a)^3 + \dots$$



System Identification

Complex Number and Taylor Series Review

- Real and imaginary parts
- Euler's formula

$$e^{ix} = \cos x + i \sin x$$

- Can be expressed with magnitude and phase

$$z = r(\cos \varphi + i \sin \varphi)$$



- Rules of multiplication and division

$$z_1 z_2 = r_1 r_2 (\cos(\varphi_1 + \varphi_2) + i \sin(\varphi_1 + \varphi_2))$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} (\cos(\varphi_1 - \varphi_2) + i \sin(\varphi_1 - \varphi_2))$$

- Taylor series definition
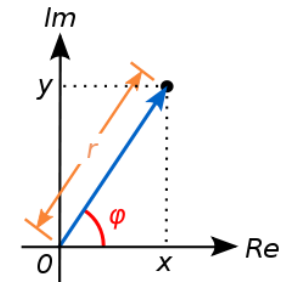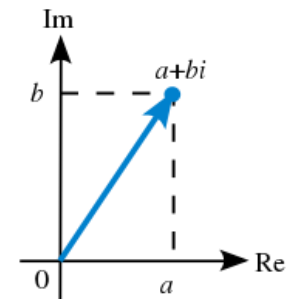
$$\sum_{n=0}^{\infty} \frac{f^{(n)}(a)}{n!} (x-a)^n = f(a) + \frac{f'(a)}{1!} (x-a) + \frac{f''(a)}{2!} (x-a)^2 + \frac{f'''(a)}{3!} (x-a)^3 + \dots$$



System Identification

Derivation of Euler's Formula with Taylor Series


$$z = x + iy = |z|(\cos \varphi + i \sin \varphi) = re^{i\varphi}$$

$$e^{ix} = 1 + ix + \frac{(ix)^2}{2!} + \frac{(ix)^3}{3!} + \frac{(ix)^4}{4!} + \frac{(ix)^5}{5!} + \frac{(ix)^6}{6!} + \frac{(ix)^7}{7!} + \frac{(ix)^8}{8!} + \dots$$

$$= 1 + ix - \frac{x^2}{2!} - \frac{ix^3}{3!} + \frac{x^4}{4!} + \frac{ix^5}{5!} - \frac{x^6}{6!} - \frac{ix^7}{7!} + \frac{x^8}{8!} + \dots$$

$$= \left(1 - \frac{x^2}{2!} + \frac{x^4}{4!} - \frac{x^6}{6!} + \frac{x^8}{8!} - \dots\right) + i \left(x - \frac{x^3}{3!} + \frac{x^5}{5!} - \frac{x^7}{7!} + \dots\right)$$

$$= \cos x + i \sin x .$$

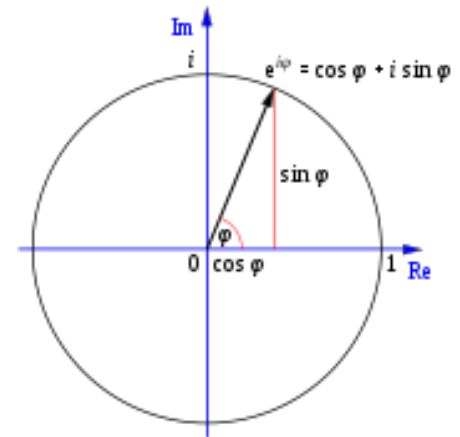



$$e^{i\pi} + 1 = 0$$

System Identification

Impulse and Step Function

- Idealized function for analysis
- Unit impulse function (Dirac Delta function) denoted as $\delta(t-a)$
- Unit step function (Heaviside step function) denoted as $u(t-a)$
- The derivative of $u(t-a)$ is $\delta(t-a)$
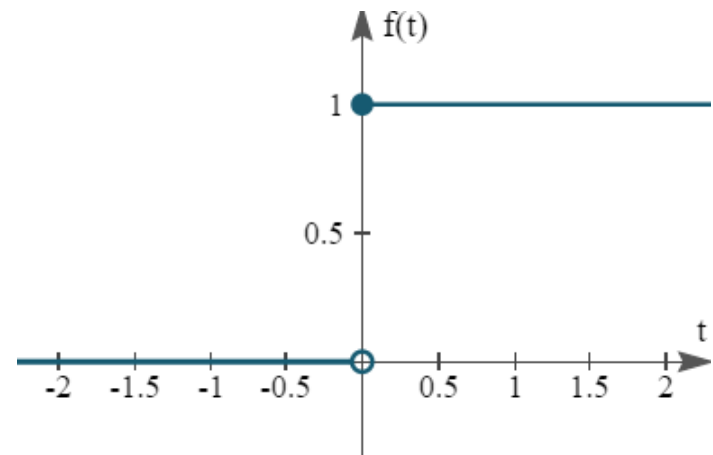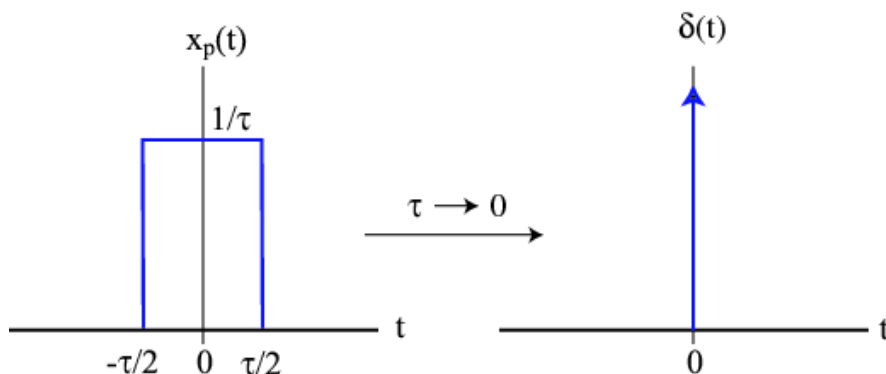
$$\int_{-\infty}^{\infty} \delta(t) dt = \lim_{\Delta \rightarrow 0} [\Delta \cdot 1/\Delta] = 1$$



System Identification

Impulse Response and Convolution


- System response to an impulse function
- Any signal can be decomposed by impulse signal
- Convolution of input yields actual response

$$\delta_{\Delta}(t) = \begin{cases} 1/\Delta & 0 \leq t < \Delta \\ 0 & \text{else} \end{cases} \quad \delta(t) \triangleq \lim_{\Delta \rightarrow 0} \delta_{\Delta}(t) = \begin{cases} \infty & t = 0 \\ 0 & \text{else} \end{cases}$$

$$x(t) \approx \sum_{m=-\infty}^{\infty} x(m\Delta) \delta_{\Delta}(t - m\Delta) \Delta$$

$$x(t) = \lim_{\Delta \rightarrow 0} \sum_{m=-\infty}^{\infty} x(m\Delta) \delta_{\Delta}(t - m\Delta) \Delta = \int_{-\infty}^{\infty} x(\tau) \delta(t - \tau) d\tau$$
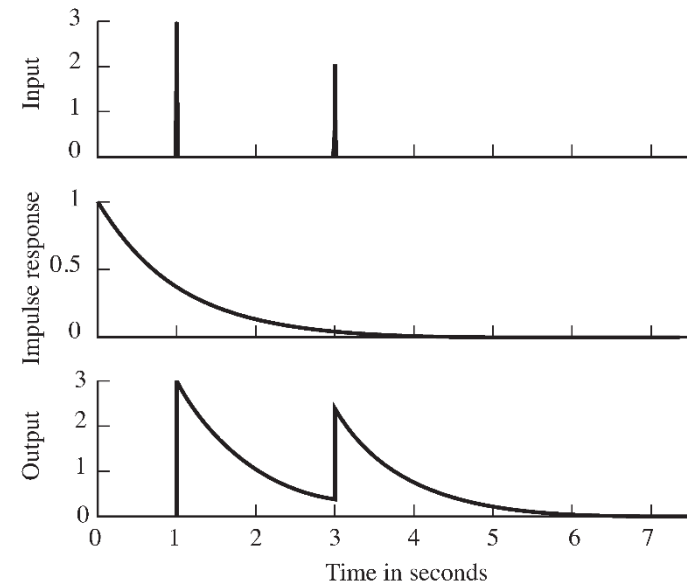
$$\begin{aligned} y(t) &= \mathcal{O}[x(t)] = \mathcal{O}\left[\int_{-\infty}^{\infty} x(\tau) \delta(t - \tau) d\tau\right] \\ &= \int_{-\infty}^{\infty} x(\tau) \mathcal{O}[\delta(t - \tau)] d\tau = \int_{-\infty}^{\infty} x(\tau) h(t - \tau) d\tau = h(t) * x(t) \end{aligned}$$



System Identification

Fourier and Laplace Transformation

- Fourier transformation: express signal into frequency domain

$$H(\omega) = \mathcal{F}\{f(t)\} = \int_{-\infty}^{\infty} e^{-j\omega t} f(t) dt$$

- Bi-lateral Laplace transformation:

$$G(s) = \mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} e^{-st} f(t) dt$$

- Use unilateral for casual system
- Use Laplace for simplicity
- Laplace transformation of derivative:



$$\mathcal{L}\left(\frac{df(t)}{dt}\right) = \int_{0^-}^{\infty} \frac{df(t)}{dt} e^{-st} dt$$

$$\int_a^b u \cdot dv = u \cdot v \Big|_a^b - \int_a^b v \cdot du$$

$$du = -s \cdot e^{-st} dt \quad u = e^{-st}$$

$$v = f(t) \quad dv = \frac{df(t)}{dt} dt$$

$$\int_{0^-}^{\infty} \frac{df(t)}{dt} e^{-st} dt = \left[e^{-st} \cdot f(t) \right]_{0^-}^{\infty} - \int_{0^-}^{\infty} f(t) \cdot (-s) \cdot e^{-st} dt$$

$$= \left[e^{-st} \cdot f(\infty) - e^{-0^-t} \cdot f(0^-) \right] + s \int_{0^-}^{\infty} f(t) \cdot e^{-st} dt$$

$$\int_{0^-}^{\infty} \frac{df(t)}{dt} e^{-st} dt = \left[\cancel{e^{-st} \cdot f(\infty)} - \cancel{e^{-0^-t} \cdot f(0^-)} \right] + sF(s) = \boxed{sF(s) - f(0^-)}$$

System Identification

The Convolution Theorem

- For causal system, use unilateral Laplace transformation

$$\mathcal{UL}[x(t)] = X(s) \triangleq \int_{-\infty}^{\infty} x(t)u(t)e^{-st}dt = \int_{0^-}^{\infty} x(t)e^{-st}dt$$

- Prove that convolution becomes multiplication

$$L[f * g] = L[f] \cdot L[g] = F \cdot G$$

$$L[f * g] = L[f] \cdot L[g] = F \cdot G$$

$$\text{Proof: } F(s) \cdot G(s) = F(s) \int_0^{\infty} e^{-st} g(t) dt = \int_0^{\infty} F(s) e^{-s\tau} g(\tau) d\tau$$

$$e^{-s\tau} F(s) = L[H(t-\tau)f(t-\tau)]$$

$$F(s) \cdot G(s) = \int_0^{\infty} L[H(t-\tau)f(t-\tau)]g(\tau)d\tau$$

$$= \int_0^{\infty} \left[\int_0^{\infty} e^{-st} H(t-\tau)f(t-\tau)dt \right] g(\tau)d\tau$$

$$= \int_0^{\infty} \int_0^{\infty} e^{-st} g(\tau) H(t-\tau)f(t-\tau)dt d\tau$$

$$= \int_0^{\infty} \int_{\tau}^{\infty} e^{-st} g(\tau) f(t-\tau)dt d\tau$$



$$= \int_0^{\infty} \int_0^t e^{-st} g(\tau) f(t-\tau) d\tau dt = \int_0^{\infty} e^{-s\tau} \left[\int_0^t g(\tau) f(t-\tau) d\tau \right] dt$$

$$= \int_0^{\infty} e^{-st} (f * g)(t) dt = L[f * g](s)$$


System Identification

Switching Domain for Analysis


- Signals are convoluted when going through a system

$$(f * g)(t) \stackrel{\text{def}}{=} \int_{-\infty}^{\infty} f(\tau)g(t - \tau) d\tau$$

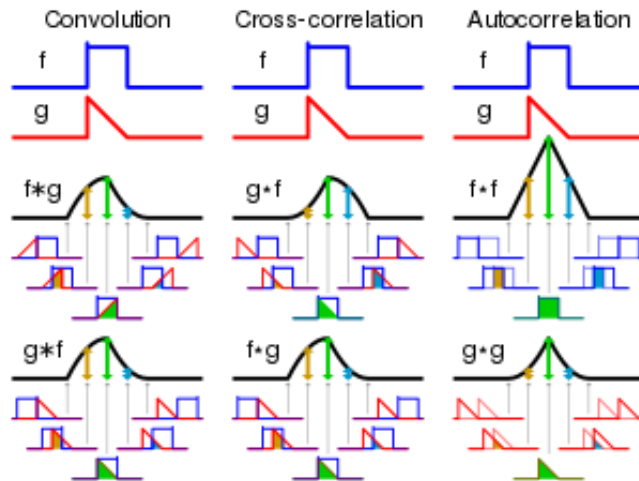- Multiplications is a lot easier than convolution



Time domain

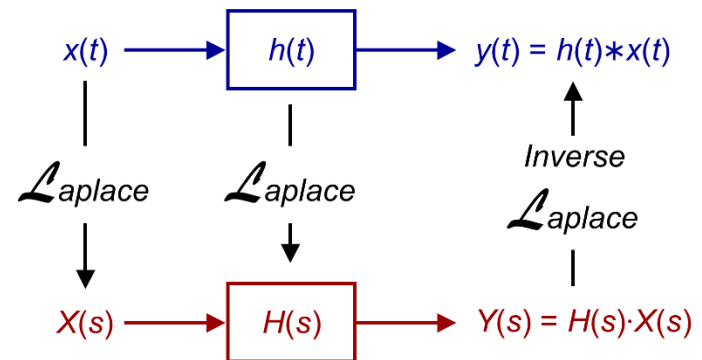

Frequency domain

System Identification

Laplace Transformation Table

- Laplace transformation simplifies the analysis process for ODES
- Easy representation
- Solving with partial fraction expansion and lookup tables
- Definition

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

First Derivative	$\frac{df(t)}{dt} \xrightarrow{L} sF(s) - f(0^-)$
Second Derivative	$\frac{d^2 f(t)}{dt^2} \xrightarrow{L} s^2 F(s) - sf(0^-) - \dot{f}(0^-)$

Common Laplace Transform Pairs


Time Domain Function		Laplace Domain Function
Name	Definition*	
Unit Impulse	$\delta(t)$	1
Unit Step	$\gamma(t)^\dagger$	$\frac{1}{s}$
Unit Ramp	t	$\frac{1}{s^2}$
Parabola	t^2	$\frac{2}{s^3}$
Exponential	e^{-at}	$\frac{1}{s+a}$
Asymptotic Exponential	$\frac{1}{a}(1 - e^{-at})$	$\frac{1}{s(s+a)}$
Dual Exponential	$\frac{1}{b-a}(e^{-at} - e^{-bt})$	$\frac{1}{(s+a)(s+b)}$
Asymptotic Dual Exponential	$\frac{1}{ab}\left[1 + \frac{1}{a-b}(be^{-at} - ae^{-bt})\right]$	$\frac{1}{s(s+a)(s+b)}$
Time multiplied Exponential	te^{-at}	$\frac{1}{(s+a)^2}$
Sine	$\sin(\omega_0 t)$	$\frac{\omega_0}{s^2 + \omega_0^2}$
Cosine	$\cos(\omega_0 t)$	$\frac{s}{s^2 + \omega_0^2}$
Decaying Sine	$e^{-at} \sin(\omega_0 t)$	$\frac{\omega_0}{(s+a)^2 + \omega_0^2}$
Decaying Cosine	$e^{-at} \cos(\omega_0 t)$	$\frac{s+a}{(s+a)^2 + \omega_0^2}$
Generic Oscillatory Decay	$e^{-at}\left[B\cos(\omega_0 t) + \frac{C-aB}{\omega_0}\sin(\omega_0 t)\right]$	$\frac{Bs+C}{(s+a)^2 + \omega_0^2}$
Prototype Second Order Lowpass, underdamped	$\frac{\omega_0}{\sqrt{1-\zeta^2}}e^{-\zeta\omega_0 t}\sin(\omega_0\sqrt{1-\zeta^2}t)$	$\frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$
Prototype Second Order Lowpass, underdamped Step Response	$1 - \frac{1}{\sqrt{1-\zeta^2}}e^{-\zeta\omega_0 t}\sin(\omega_0\sqrt{1-\zeta^2}t + \phi)$ $\phi = \tan^{-1}\left(\frac{\sqrt{1-\zeta^2}}{\zeta}\right)$	$\frac{\omega_0^2}{s(s^2 + 2\zeta\omega_0 s + \omega_0^2)}$

System Identification

RLC Circuit Impedance Transfer Function

- Model system using impedance form
- Utilize series and parallel connection
- Obtain the result in transfer function form
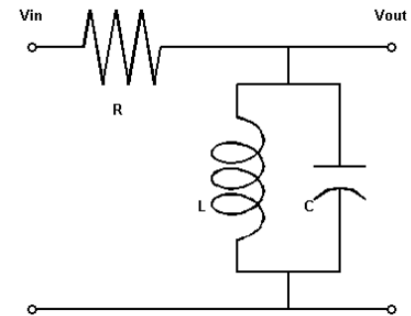
$$G(s) = \frac{s/(RC)}{s^2 + s/(RC) + 1/(LC)}$$



- What is a transfer function
 - Linear time-invariant system can be represented by Bode plot
 - Mathematically: Zero initial condition unilateral Laplace transformation

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

- Characterize frequency response for amplitude and phase

System Identification

RLC Circuit Bode Plot

- Characterize AC frequency response of system
- Convert to Fourier transform by setting $s = j\omega$
- Obtain amplitude and phase

$$\begin{aligned} u(t) &= \sin(\omega t) \\ y(t) &= y_0 \sin(\omega t + \varphi) \\ y_0 &= |H(j\omega)| \\ \varphi &= \arg H(j\omega) \end{aligned}$$

- Gain expressed in dB


$$G_{dB} = 20 \log_{10} \left(\frac{V}{V_0} \right) \text{ dB}$$

- With $R = 1$, $C = 1$, $L = 1$

$$G(s) = \frac{s/(RC)}{s^2 + s/(RC) + 1/(LC)}$$

$$G(s) = \mathcal{L}\{f(t)\} = \int_{-\infty}^{\infty} e^{-st} f(t) dt$$
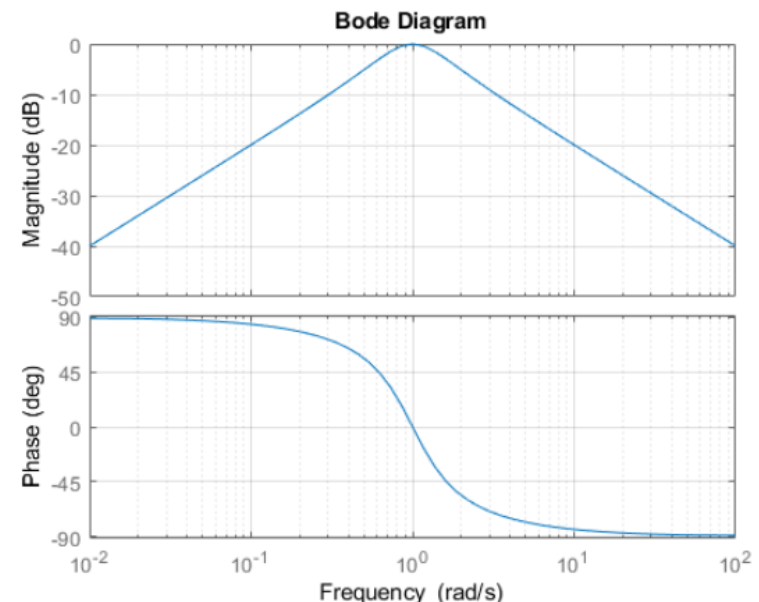
$$H(\omega) = \mathcal{F}\{f(t)\} = \int_{-\infty}^{\infty} e^{-j\omega t} f(t) dt$$



Bode plot for RLC Circuit

System Identification

Things to Remember

- A system can be described in many ways
 - Model and parameter values
 - Unit impulse response
 - Unit step response (will appear later)
 - Frequency response (Bode plot)
- A signal can be decomposed with many impulse or sine functions
- Signal going through a system is being convoluted
- We use the unilateral Laplace transformation to make our life easier

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

- We will revisit these concepts in the section of controls

System Identification

Methods for Frequency Response


- Bode plot can be experimentally measured by conducting a frequency sweep with a dynamic signal analyzer, which is a time consuming but reliable procedure.
- Advanced system identification procedure using binary stochastic signal input to simultaneously excite a broad band of signal and obtain bode plot using Fourier transformation and power spectral density functions is also available.



System Identification

Dynamic Signal Analyzer

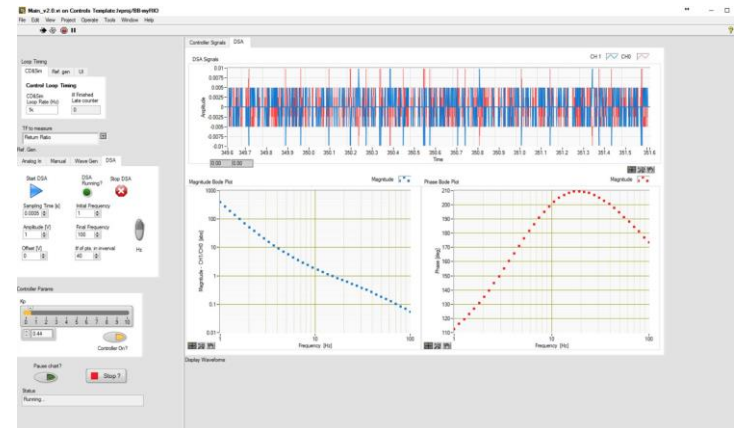
- Conduct frequency sweep automatically to obtain bode plot
- Implementation in LabVIEW available



System Identification

Random Binary Stochastic Signal

- The transfer function of a system can be obtained by the output power spectrum divided by the input power spectrum for amplitude and phase estimation
- The input can be generated by filtering a Gaussian white noise to focus on the frequency of interest
- A Random Binary Stochastic (RBS) signal can be useful for system ID when only digital excitation is available
- RBS signal system ID saves time in general but can be challenging when a controller is in the loop

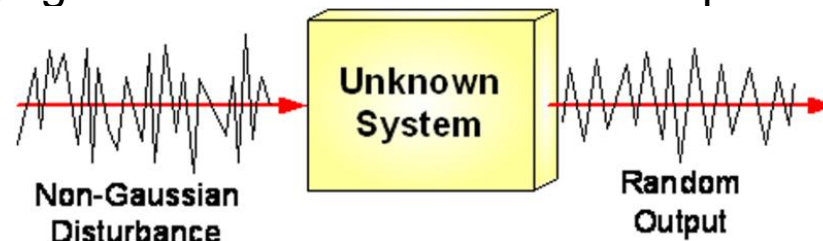



Thank You!